

Computer Organization & Architecture Lab

Paper Code: PCCCS492

Work Book



Department of Computer Science & Engineering

B. Tech

2nd year 4th Semester

NAME: Aditya Bose

SECTION: A

CLASS ROLL NO.: 1

ENROLLMENT NO.: 12020002002001

INSTITUTE OF ENGINEERING & MANAGEMENT

COMPUTER ARCHITECTURE LAB

PAPER CODE: PCCCS 492

LAB ASSIGNMENTS

- 1.Implementation of AND, OR, NOT, XOR, NANAD, NOR gates using Xilinx ISE.**
- 2. Implementation of Half Adder, Half Subtractor, Full Adder, Full Subtractor using Xilinx ISE.**
- 3. Implementation of 8 bit Adder, 8bit Subtractor, 8 bit Multiplier and 4 bit parallel Adder and 4 bit parallel subtractor using Xilinx ISE.**
- 4. Implementation of Binary to Gray and Gray to binary using Xilinx ISE.**
- 5. Implementation of 4 bit comparator, 2:4 Decoder, 3:8 Decoder using Xilinx ISE.**
- 6. Implementation of 2:4 Decoder (using case), 4:2 Encoder (Data flow and using case), 8:3 Encoder (using Loop).**
- 7. Implementation of 2:1 MUX (Data flow), 4:1 MUX (Dataflow, if-else, using case), 1:4 DEMUX (using case and data flow) using Xilinx ISE.**
- 8. Implementation of Full Adder using Half Adders (Structural Method), 4 bit Parallel Adder (using Structural Method).**
- 9. Implementation of 2:1 MUX using basic gates(Structural Method), 4:1 MUX using 2:1 MUX (using Structural Method).**
- 10. Implementation of SR Flip-Flop, JK Flip Flop, D Flip Flop and T (Toggle) Flip Flop using Xilinx ISE.**

Computer Architecture Laboratory Projects (PCCCS 492)

- 1 Design Control Unit (CU) based on 8-bit word size processor. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 2 Design Arithmetic & Logical Unit(CU) based on 8-bit word size processor.(CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 3 Design a Signed Multiplier Unit. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 4 Design a *Customized* Encrypter with key size of 4-bit. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 5 Design a *Customized* Decrypter with key size of 4-bit. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 6 Design a 16-bit Cyclic Redundancy Code Checker. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 7 Design a Hamming Code Generator Unit. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 8 Design a Digital Clock Unit with HH:MM:SS output. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 9 Design a Stack Unit with Memory Control. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 10 Design a Instruction Queue Unit of word size n . (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 11 Design a Register Unit which contains x number of registers (x is a multiple of 2). It must allow register pair operations. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)
- 12 Design Memory (RAM) Unit with n word-size & m number of words. (CO1, CO2, CO3, CO4, PO1-PO5, PO9, PO12)

Assignment 1: Implementation of AND, OR, NOT, XOR, NAND, NOR gates using Xilinx ISE.

Aim:

Objective: To implement OR gate

Software used:

Property Name	Xilinx ISE
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	VHDL

Theory:

OR gate is a logical circuit which performs the logical OR operation on 2 or more Boolean variables.

Truth Table:

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Behavioral Model:

Here, the gate is designed, using the **truth table**. It simulates the behavior of the output of the gate, upon taking different Boolean variables as inputs. The **Behavioral Architecture** is used in this case.

Data flow Model:

Here, the gate is constructed, using the **Dataflow Architecture**. The gate is designed, using it's **Boolean function**.

Code:

1. Behavioral Model Code:

```
-- Code your testbench here
library IEEE;
use IEEE.std_logic_1164.all;

entity tb_OR_gate is
end tb_OR_gate;

architecture behavior of tb_OR_gate is
  component OR_gate is
    port(x: in std_logic;
         y: in std_logic;
         z: out std_logic;
        );
  end component;
  signal x,y: std_logic := '0';
  signal z: std_logic;

begin
```

```

uut: OR_gate port map(x,y,z);

stim: process
begin
  x<='0';y<='0'; wait for 100 ns;
  x<='0';y<='1'; wait for 100 ns;
  x<='1';y<='0'; wait for 100 ns;
  x<='1';y<='1'; wait for 100 ns;
end process;
end;

-- Code your design here
library IEEE;
use IEEE.std_logic_1164.all;

entity OR_gate is
  port(x: in std_logic;
        y: in std_logic;
        z: out std_logic;
        );
end OR_gate;

architecture Behavioral of OR_gate is
begin
  process(x,y)

    begin

      if(x='0' and y='0') then z<='0';
      else z<='1';
      end if;

    end process;
end Behavioral;

```

2. Data flow Model Code

```

-- Code your testbench here

library IEEE;

```

```

use IEEE.std_logic_1164.all;

entity tb_OR_gate is
end tb_OR_gate;

architecture myarch of tb_OR_gate is
    component OR_gate is
        port(a: in std_logic;
              b: in std_logic;
              c: out std_logic;
              );
    end component;
    signal a,b: std_logic:='0';
    signal c: std_logic;
begin
    uut: OR_gate port map(a,b,c);

    stim: process
    begin
        a<='0';b<='0'; wait for 100 ns;
        a<='0';b<='1'; wait for 100 ns;
        a<='1';b<='0'; wait for 100 ns;
        a<='1';b<='1'; wait for 100 ns;
    end process;
end myarch;

```

-- Code your design here

library IEEE;

use IEEE.std_logic_1164.all;

entity OR_gate is

port(a: in std_logic;

b: in std_logic;

c: out std_logic;

);

end OR_gate;


architecture myarch of OR_gate is

begin

c<=a or b;

end myarch;

Output:

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Objective: To implement AND gate

Software used:

Property Name	Xilinx ISE
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	VHDL

Theory:

The **AND Gate** performs the **logical AND** operation, between 2 or more different Boolean variables. It simulates the **arithmetic multiplication operation**.

Truth Table:

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	0

1	0	0
1	1	1

Behavioral Model:

Here, the gate is designed, using the **truth table**. It simulates the behavior of the output of the gate, upon taking different Boolean variables as inputs. The **Behavioral Architecture** is used in this case.

Data flow Model:

Here, the gate is constructed, using the **Dataflow Architecture**. The gate is designed, using it's **Boolean function**.

Code:

1.Behavioral Model Code:

```
-- Code your testbench here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity tb_AND_gate is
```

```
end tb_AND_gate;
```

```
architecture behavior of tb_AND_gate is
```

```
    component AND_gate is
```

```
        port(x: in std_logic;
```

```
             y: in std_logic;
```

```
             z: out std_logic;
```

```

    );

end component;

signal x,y: std_logic := '0';

signal z: std_logic;

begin

    uut: AND_gate port map(x,y,z);


stim: process
begin
    x<='0';y<='0'; wait for 100 ns;
    x<='0';y<='1'; wait for 100 ns;
    x<='1';y<='0'; wait for 100 ns;
    x<='1';y<='1'; wait for 100 ns;
end process;

end;


-- Code your design here

library IEEE;

use IEEE.std_logic_1164.all;


entity AND_gate is
    port(x: in std_logic;
         y: in std_logic;
         z: out std_logic;

    );

```

```
end AND_gate;
```

architecture Behavioral of AND_gate is

```
begin
```

```
process(x,y)
```

```
begin
```

```
if(x='1' and y='1') then z<='1';
```

```
else z<='0';
```

```
end if;
```

```
end process;
```

```
end Behavioral;
```

2. Data flow Model Code:

```
-- Code your testbench here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity tb_AND_gate is
```

```
end tb_AND_gate;
```

```
architecture myarch of tb_AND_gate is
```

```
component AND_gate is
```

```

port(a: in std_logic;
      b: in std_logic;
      c: out std_logic;
    );
end component;

signal a,b: std_logic:='0';
signal c: std_logic;

begin

uut: AND_gate port map(a,b,c);


stim: process
begin
  a<='0';b<='0'; wait for 100 ns;
  a<='0';b<='1'; wait for 100 ns;
  a<='1';b<='0'; wait for 100 ns;
  a<='1';b<='1'; wait for 100 ns;
end process;

end myarch;


-- Code your design here

library IEEE;
use IEEE.std_logic_1164.all;


entity AND_gate is
port(a: in std_logic;
      b: in std_logic;

```

```
c: out std_logic;  
  
);  
end AND_gate;
```


architecture myarch of AND_gate is

```
begin
```

```
c<=a and b;
```

```
end myarch;
```

Output:

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Objective: To implement NOT gate

Software used:

Property Name	Xilinx ISE
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	VHDL

Theory:

The **NOT Gate** inverts a Boolean variable, i.e., alters its value from 0 to 1 and from 1 to 0. Thus, it performs the **logical NOT** operation, on one Boolean variable.

Truth Table:

INPUT	OUTPUT
A	Y
0	1
1	0

Behavioral Model:

Here, the gate is designed, using the **truth table**. It simulates the behavior of the output of the gate, upon taking different Boolean variables as inputs. The **Behavioral Architecture** is used in this case.

Data flow Model:

Here, the gate is constructed, using the **Dataflow Architecture**. The gate is designed, using it's **Boolean function**.

Code:

1. Behavioral Model Code:

```
entity tb_NOT_gate is
```

```
end tb_NOT_gate;
```

```
architecture behavior of tb_NOT_gate is
```

```
    component NOT_gate is
```

```
        port(x: in std_logic;
```

```
              y: out std_logic;
```

```
        );
```

```
    end component;
```

```
    signal x: std_logic := '0';
```

```
    signal y: std_logic;
```

```
begin
```

```
    uut: NOT_gate port map(x,y);
```

```
stim: process
```

```
begin
```

```
    x<='0'; wait for 100 ns;
```

```
    x<='1'; wait for 100 ns;
```

```
end process;
```

```
end;
```

```
-- Code your design here
```



```

library IEEE;

use IEEE.std_logic_1164.all;

entity NOT_gate is
    port(x: in std_logic;
         y: out std_logic;
         );
end NOT_gate;

architecture Behavioral of NOT_gate is
begin
    process(x)

        begin

            if(x='0') then y<='1';
            else y<='0';
            end if;

        end process;
    end Behavioral;

```

2. Data flow Model Code:

```
-- Code your testbench here
```

```

library IEEE;

use IEEE.std_logic_1164.all;

entity tb_NOT_gate is
end tb_NOT_gate;

architecture myarch of tb_NOT_gate is
    component NOT_gate is
        port(a: in std_logic;
              b: out std_logic;
              );
    end component;
    signal a: std_logic:= '0';
    signal b: std_logic;
begin
    uut: NOT_gate port map(a,b);

    stim: process
    begin
        a<='0'; wait for 100 ns;
        a<='1'; wait for 100 ns;
    end process;
end myarch;

-- Code your design here

library IEEE;

```

```
use IEEE.std_logic_1164.all;
```

entity NOT_gate is

```
port(a: in std_logic;
```

```
      b: out std_logic;
```

```
);
```

```
end NOT_gate;
```


architecture myarch of NOT_gate is

```
begin
```

```
    b<=not a;
```

```
end myarch;
```

Output:

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Objective: To implement NOR gate

Software used:

Property Name	Xilinx ISE
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	VHDL

Theory:

The **NOR Gate** represents a **NOT Gate**, followed by an **OR Gate**, i.e., it negates the OR Gate, for 2 or more Boolean variables.

Truth Table:

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Behavioral Model:

Here, the gate is designed, using the **truth table**. It simulates the behavior of the output of the gate, upon taking different Boolean variables as inputs. The **Behavioral Architecture** is used in this case.

Data flow Model:

Here, the gate is constructed, using the **Dataflow Architecture**. The gate is designed, using it's **Boolean function**.

Code:

1.Behavioral Model Code:

-- Code your testbench here

library IEEE;

use IEEE.std_logic_1164.all;

entity tb_NOR_gate is

end tb_NOR_gate;

architecture behavior of tb_NOR_gate is

component NOR_gate is

port(x: in std_logic;

 y: in std_logic;

 z: out std_logic;

);

end component;

signal x,y: std_logic := '0';

signal z: std_logic;

begin

uut: NOR_gate port map(x,y,z);

```
stim: process
begin
    x<='0';y<='0'; wait for 100 ns;
    x<='0';y<='1'; wait for 100 ns;
    x<='1';y<='0'; wait for 100 ns;
    x<='1';y<='1'; wait for 100 ns;
end process;
end;
```

-- Code your design here

```
library IEEE;
use IEEE.std_logic_1164.all;
```

```
entity NOR_gate is
port(x: in std_logic;
     y: in std_logic;
     z: out std_logic;
);
end NOR_gate;
```

architecture Behavioral of NOR_gate is

```
begin
    process(x,y)
```

```
begin
```

```
if(x='0' and y='0') then z<='1';
```

```
else z<='0';
```

```
end if;
```

```
end process;
```

```
end Behavioral;
```

2.Data flow Model Code:

```
-- Code your testbench here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity tb_NOR_gate is
```

```
end tb_NOR_gate;
```

```
architecture myarch of tb_NOR_gate is
```

```
component NOR_gate is
```

```
port(a: in std_logic;
```

```
      b: in std_logic;
```

```
      c: out std_logic;
```

```
);
```

```
end component;
```

```
signal a,b: std_logic:='0';
```

```
signal c: std_logic;
```

```
begin
```

```
uut: NOR_gate port map(a,b,c);
```

```
stim: process
```

```
begin
```

```
a<='0';b<='0'; wait for 100 ns;
```

```
a<='0';b<='1'; wait for 100 ns;
```

```
a<='1';b<='0'; wait for 100 ns;
```

```
a<='1';b<='1'; wait for 100 ns;
```

```
end process;
```

```
end myarch;
```

```
-- Code your design here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity NOR_gate is
```

```
port(a: in std_logic;
```

```
      b: in std_logic;
```

```
      c: out std_logic;
```

```
);
```

```
end NOR_gate;
```


```
architecture myarch of NOR_gate is
```

```
begin
```

```
c<=a nor b;
```


end myarch;

Output:

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Objective: To implement NAND gate

Software used:

Property Name	Xilinx ISE
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	VHDL

Theory:

The **NAND Gate** represents an AND Gate, followed by a NOT Gate. It negates the logical AND operation, for 2 or more Boolean variables.

Truth Table:

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Behavioral Model:

Here, the gate is designed, using the **truth table**. It simulates the behavior of the output of the gate, upon taking different Boolean variables as inputs. The **Behavioral Architecture** is used in this case.

Data flow Model:

Here, the gate is constructed, using the **Dataflow Architecture**. The gate is designed, using it's **Boolean function**.

Code:

1. Behavioral Model Code:

-- Code your testbench here

library IEEE;

use IEEE.std_logic_1164.all;

entity tb_NAND_gate is

end tb_NAND_gate;

architecture behavior of tb_NAND_gate is

component NAND_gate is

port(x: in std_logic;

 y: in std_logic;

 z: out std_logic;

);

end component;

signal x,y: std_logic := '0';

signal z: std_logic;

begin

```
 uut: NAND_gate port map(x,y,z);
```

```
stim: process
```

```
begin
```

```
  x<='0';y<='0'; wait for 100 ns;
```

```
  x<='0';y<='1'; wait for 100 ns;
```

```
  x<='1';y<='0'; wait for 100 ns;
```

```
  x<='1';y<='1'; wait for 100 ns;
```

```
end process;
```

```
end;
```

```
-- Code your design here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity NAND_gate is
```

```
  port(x: in std_logic;
```

```
        y: in std_logic;
```

```
        z: out std_logic;
```

```
  );
```

```
end NAND_gate;
```

```
architecture Behavioral of NAND_gate is
```

```
begin
```

```
  process(x,y)
```

```
begin
```

```
    if(x='1' and y='1') then z<='0';
```

```
    else z<='1';
```

```
end if;
```

```
end process;
```

```
end Behavioral;
```

2. Data flow Model Code:

```
-- Code your testbench here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity tb_NAND_gate is
```

```
end tb_NAND_gate;
```

```
architecture myarch of tb_NAND_gate is
```

```
    component NAND_gate is
```

```
        port(a: in std_logic;
```

```
              b: in std_logic;
```

```
              c: out std_logic;
```

```
        );
```

```
    end component;
```

```
    signal a,b: std_logic:= '0';
```

```
signal c: std_logic;

begin

uut: NAND_gate port map(a,b,c);
```

```
stim: process
begin
    a<='0';b<='0'; wait for 100 ns;
    a<='0';b<='1'; wait for 100 ns;
    a<='1';b<='0'; wait for 100 ns;
    a<='1';b<='1'; wait for 100 ns;
end process;
end myarch;
```

```
-- Code your design here
```

```
library IEEE;
use IEEE.std_logic_1164.all;
```

```
entity NAND_gate is
```

```
port(a: in std_logic;
      b: in std_logic;
      c: out std_logic;
    );
```

```
end NAND_gate;
```


```
architecture myarch of NAND_gate is
```

```
begin
```

```
c<=a nand b;
```

```
end myarch;
```

Output:

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Objective: To implement XOR gate

Software used:

Property Name	Xilinx ISE
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	VHDL

Theory:

This gate is used to implement the logical XOR operation, between 2 or more Boolean variables. It produces an output 1 when the values of the variables are different and 0 when they are the equal.

Truth Table:

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Behavioral Model:

Here, the gate is designed, using the **truth table**. It simulates the behavior of the output of the gate, upon taking different Boolean variables as inputs. The **Behavioral Architecture** is used in this case.

Data flow Model:

Here, the gate is constructed, using the **Dataflow Architecture**. The gate is designed, using it's **Boolean function**.

Code:

1. Behavioral Model Code:

-- Code your testbench here

library IEEE;

use IEEE.std_logic_1164.all;

entity tb_XOR_gate is

end tb_XOR_gate;

architecture behavior of tb_XOR_gate is

component XOR_gate is

port(x: in std_logic;

 y: in std_logic;

 z: out std_logic;

);

end component;

signal x,y: std_logic := '0';

signal z: std_logic;

begin

uut: XOR_gate port map(x,y,z);

```

stim: process
begin
    x<='0';y<='0'; wait for 100 ns;
    x<='0';y<='1'; wait for 100 ns;
    x<='1';y<='0'; wait for 100 ns;
    x<='1';y<='1'; wait for 100 ns;
end process;
end;

-- Code your design here

library IEEE;
use IEEE.std_logic_1164.all;

entity XOR_gate is
port(x: in std_logic;
     y: in std_logic;
     z: out std_logic;
    );
end XOR_gate;

architecture Behavioral of XOR_gate is
begin
    process(x,y)

    begin

```

```
if(x=y) then z<='0';  
else z<='1';  
end if;
```

```
end process;  
end Behavioral;
```

2.Data flow Model Code:

```
-- Code your testbench here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity tb_XOR_gate is
```

```
end tb_XOR_gate;
```

```
architecture myarch of tb_XOR_gate is
```

```
component XOR_gate is
```

```
port(a: in std_logic;
```

```
      b: in std_logic;
```

```
      c: out std_logic;
```

```
);
```

```
end component;
```

```
signal a,b: std_logic:= '0';
```

```
signal c: std_logic;
```

```
begin
```

```
 uut: XOR_gate port map(a,b,c);
```

```
stim: process
```

```
begin
```

```
  a<='0';b<='0'; wait for 100 ns;
```

```
  a<='0';b<='1'; wait for 100 ns;
```

```
  a<='1';b<='0'; wait for 100 ns;
```

```
  a<='1';b<='1'; wait for 100 ns;
```

```
end process;
```

```
end myarch;
```

```
-- Code your design here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity XOR_gate is
```

```
  port(a: in std_logic;
```

```
        b: in std_logic;
```

```
        c: out std_logic;
```

```
  );
```

```
end XOR_gate;
```


```
architecture myarch of XOR_gate is
```

```
begin
```

```
  c<=a xor b;
```

```
end myarch;
```

Output:

 

Discussion :

Assignment:2 Implementation of Half Adder, Half Subtractor, Full Adder, Full Subtractor using Xilinx ISE.

Aim:

Software used:

Property Name	Xilinx ISE
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	VHDL

Half adder:

Theory:

The **half-adder** is a type of electronic circuit, that is able to add 2 binary digits (of size 1 bit each) and provide the output along with the carry value. The expressions for the sum and carry bits are as follows:-

- **Sum:** $S = A \text{ XOR } B$
- **Carry:** $C = A \text{ AND } B$

Truth table:

INPUT		OUTPUT	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Behavioral Model:

Here, the circuit is designed using the **truth table**. The **Behavioral Architecture** is used in this case, which simulates the output behaviour of the circuit, considering various inputs.

Data flow Model:

Here, the circuit is designed using the **Dataflow Architecture**, which takes into account, the **Boolean function**, of the circuit.

Code:

1. Behavioral Model Code:

```
-- Code your testbench here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity tb_HALF_adder is
```

```
end tb_HALF_adder;
```

```
architecture behavior of tb_HALF_adder is
```

```
    component HALF_adder is
```

```
        port(a: in std_logic;
```

```
              b: in std_logic;
```

```
              s: out std_logic;
```

```
              c: out std_logic;
```

```
        );
```

```
    end component;
```

```

signal x,y: std_logic := '0';
signal s,c: std_logic;

begin

uut: HALF_adder port map(x,y,s,c);

stim: process
begin
x<='0';y<='0'; wait for 100 ns;
x<='0';y<='1'; wait for 100 ns;
x<='1';y<='0'; wait for 100 ns;
x<='1';y<='1'; wait for 100 ns;
end process;
end;

-- Code your design here

library IEEE;
use IEEE.std_logic_1164.all;

entity HALF_adder is
port(a: in std_logic;
      b: in std_logic;
      s: out std_logic;
      c: out std_logic;
);
end HALF_adder;

```


architecture Behavioral of HALF_adder is

begin

process(a,b)

begin

if(a=b) then s<='0';

else s<='1';

end if;

if(a='0' and b='1') then c<='1';

else c<='0';

end if;

end process;

end Behavioral;

2.Data flow Model Code:

-- Code your testbench here

library IEEE;

use IEEE.std_logic_1164.all;

entity tb_HALF_adder is

end tb_HALF_adder;

architecture myarch of tb_HALF_adder is

component HALF_adder is

port(

a: in std_logic;

b: in std_logic;

s: out std_logic;

c: out std_logic;

);

end component;

signal a,b: std_logic := '0';

signal s,c: std_logic;

begin

uut: HALF_adder port map(a,b,s,c);

stim: process

begin

a<='0';b<='0'; wait for 100 ns;

a<='0';b<='1'; wait for 100 ns;

a<='1';b<='0'; wait for 100 ns;

a<='1';b<='1'; wait for 100 ns;

end process;

end myarch;

-- Code your design here

library IEEE;

use IEEE.std_logic_1164.all;

entity HALF_adder is

port(a: in std_logic;

b: in std_logic;

s: out std_logic;

c: out std_logic;

);

end HALF_adder;

architecture myarch of HALF_adder is


begin

s<=a xor b;

c<=a and b;

end myarch;

Output:

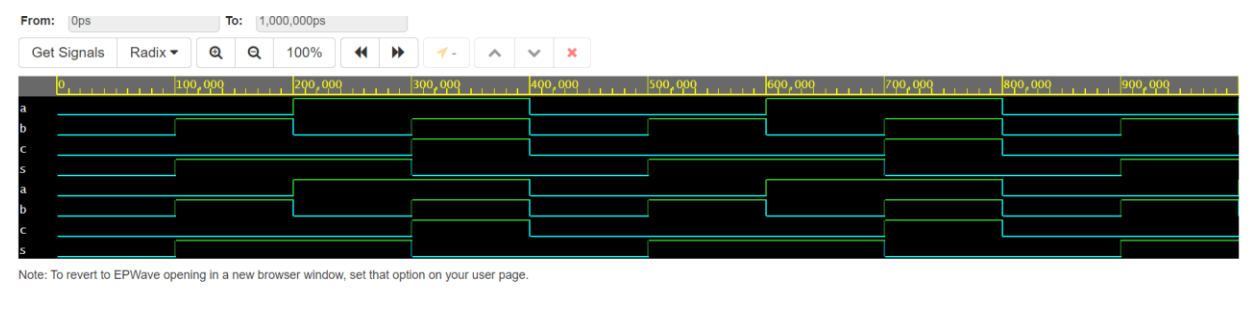

Discussion:

Half Subtractor:

Theory:

A Half Subtractor is an electronic circuit, which subtracts 2 binary digits (each of size 1 Bit) and is able to provide both difference and borrow, as outputs. The expressions for difference and borrow are as follows:

- **Difference:** $D = X \text{ XOR } Y$
- **Borrow:** $B = (\text{NOT } X) \text{ AND } Y$

Truth table:

INPUT		OUTPUT	
A	B	Difference	Bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Behavioral Model:

Here, the circuit is designed using the **truth table**. The **Behavioral Architecture** is used in this case, which simulates the output behaviour of the circuit, considering various inputs.

Data flow Model:

Here, the circuit is designed using the **Dataflow Architecture**, which takes into account, the **Boolean function**, of the circuit.

Code:

1. Behavioral Model Code:

```
-- Code your testbench here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

entity tb_HALF_subtractor is

end tb_HALF_subtractor;

architecture behavior of tb_HALF_subtractor is

component HALF_subtractor is

port(x: in std_logic;

y: in std_logic;

d: out std_logic;

b: out std_logic;

);

end component;

signal x,y: std_logic := '0';

signal d,b: std_logic;

begin

uut: HALF_subtractor port map(x,y,d,b);

stim: process

begin

x<='0';y<='0'; wait for 100 ns;

x<='0';y<='1'; wait for 100 ns;

x<='1';y<='0'; wait for 100 ns;

x<='1';y<='1'; wait for 100 ns;

end process;

end;

```

-- Code your design here

library IEEE;
use IEEE.std_logic_1164.all;

entity HALF_subtractor is
port(x: in std_logic;
     y: in std_logic;
     d: out std_logic;
     b: out std_logic;
     );
end HALF_subtractor;

architecture Behavioral of HALF_subtractor is
begin
process(x,y)

begin

if(x=y) then d<='0';
else d<='1';
end if;

if(x='0' and y='1') then b<='1';
else b<='0';
end if;

```

```
end process;  
end Behavioral;
```

2. Data flow Model Code:

```
-- Code your testbench here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity tb_HALF_subtractor is
```

```
end tb_HALF_subtractor;
```

```
architecture myarch of tb_HALF_subtractor is
```

```
component HALF_subtractor is
```

```
port(  
    x: in std_logic;  
    y: in std_logic;  
    d: out std_logic;  
    b: out std_logic;  
);  
end component;
```

```
signal x,y: std_logic :='0';
```

```
signal d,b: std_logic;
```

```
begin
```

```
uut: HALF_subtractor port map(x,y,d,b);
```

```
stim: process
```

```
begin
  x<='0';y<='0'; wait for 100 ns;
  x<='0';y<='1'; wait for 100 ns;
  x<='1';y<='0'; wait for 100 ns;
  x<='1';y<='1'; wait for 100 ns;
end process;
end myarch;
```

-- Code your design here

```
library IEEE;
use IEEE.std_logic_1164.all;
```

entity HALF_subtractor is


```
port(x: in std_logic;
      y: in std_logic;
      d: out std_logic;
      b: out std_logic;
    );
```

end HALF_subtractor;

architecture myarch of HALF_subtractor is

```
begin
  d<=x xor y;
  b<=(not x) and y;
end myarch;
```


Output:

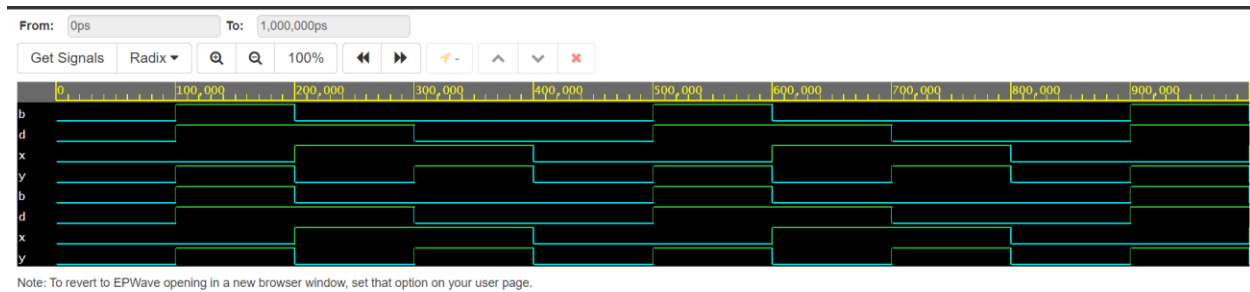

Discussion :

Full Adder:

Theory :

A **Full Adder** is an electronic circuit, which adds 3 binary digits (each of size 1 Bit) and is able to provide both the sum and carry, as outputs.

Truth table:

INPUT			OUTPUT	
A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Behavioral Model:

Here, the circuit is designed using the **truth table**. The **Behavioral Architecture** is used in this case, which simulates the output behaviour of the circuit, considering various inputs.

Data flow Model:

Here, the circuit is designed using the **Dataflow Architecture**, which takes into account, the **Boolean function**, of the circuit.

Code:

1. Behavioral Model Code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;
```

```

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity FULLADDER_BEHAVIORAL_SOURCE is
Port ( A : in  STD_LOGIC_VECTOR (2 downto 0);
      O : out  STD_LOGIC_VECTOR (1 downto 0));
end FULLADDER_BEHAVIORAL_SOURCE;

architecture Behavioral of FULLADDER_BEHAVIORAL_SOURCE is

begin

process (A)
begin

---for SUM

if (A = "001" or A = "010" or A = "100" or A = "111")
then

O(1) <= '1';

---single inverted commas used for assigning to one bit

else

O(1) < = '0';

```

```

end if;

---for CARRY

if (A = "011" or A = "101" or A = "110" or A = "111")
then

O(0) <= '1';

else

O(0) <= '0';

end if;

end process;

end Behavioral;

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity FullAdder_tb is

end entity;

```

```
architecture tb of FullAdder_tb is

component FULLADDER_BEHAVIORAL_SOURCE is

Port ( A : in STD_LOGIC_VECTOR (2 downto 0);

O : out STD_LOGIC_VECTOR (1 downto 0));

end component;


signal A : STD_LOGIC_VECTOR(2 downto 0);

signal O : STD_LOGIC_VECTOR(1 downto 0);


begin


uut: FULLADDER_BEHAVIORAL_SOURCE port map(

A => A, O => O);


stim: process

begin

A <= "000";

wait for 20 ns;
```

```
A <= "001";
```

```
wait for 20 ns;
```

```
A <= "010";
```

```
wait for 20 ns;
```

```
A <= "011";
```

```
wait for 20 ns;
```

```
A <= "100";
```

```
wait for 20 ns;
```

```
A <= "101";
```

```
wait for 20 ns;
```

```
A <= "110";
```

```
wait for 20 ns;
```

```
A <= "111";

wait for 20 ns;

wait;

end process;

end tb;
```

2. Data flow Model Code:

-- Code your testbench here

library IEEE;

use IEEE.std_logic_1164.all;

entity tb_FULL_adder is

end tb_FULL_adder;

architecture myarch of tb_FULL_adder is

component FULL_adder is

port(

a: in std_logic;

b: in std_logic;

c: in std_logic;

```

        s: out std_logic;

        cout: out std_logic;

    );

end component;

signal a,b,c: std_logic := '0';

signal s,cout: std_logic;

begin

    uut: FULL_adder port map(a,b,c,s,cout);


stim: process
begin
    a<='0';b<='0';c<='0'; wait for 100 ns;
    a<='0';b<='0';c<='1'; wait for 100 ns;
    a<='0';b<='1';c<='0'; wait for 100 ns;
    a<='0';b<='1';c<='1'; wait for 100 ns;
    a<='1';b<='0';c<='0'; wait for 100 ns;
    a<='1';b<='0';c<='1'; wait for 100 ns;
    a<='1';b<='1';c<='0'; wait for 100 ns;
    a<='1';b<='1';c<='1'; wait for 100 ns;
end process;

end myarch;


-- Code your design here

library IEEE;

use IEEE.std_logic_1164.all;

```


entity FULL_adder is

port(a: in std_logic;

b: in std_logic;

c: in std_logic;

s: out std_logic;

cout: out std_logic;

);

end FULL_adder;

architecture myarch of FULL_adder is


begin

s<=a xor b xor c;

cout<=(a and b) or (b and c) or (c and a);

end myarch;

Output:

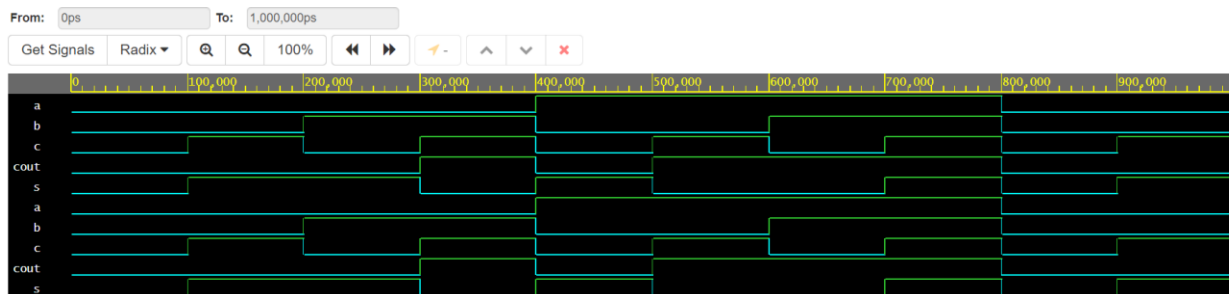

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Discussion :

Full Subtractor:

Theory :

A **Full Subtractor** is an electronic circuit, which performs the subtraction of 3 Binary digits (each of size 1 Bit) and is able to provide both the borrow and difference as the outputs.

Truth table:

INPUT			OUTPUT	
A	B	Bin	Difference	Bout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Behavioral Model:

Here, the circuit is designed using the **truth table**. The **Behavioral Architecture** is used in this case, which simulates the output behaviour of the circuit, considering various inputs.

Data flow Model:

Here, the circuit is designed using the **Dataflow Architecture**, which takes into account, the **Boolean function**, of the circuit.

Code:

1. Behavioral Model Code:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity FULLSUBTRACTOR_BEHAVIORAL_SOURCE is

Port ( A : in  STD_LOGIC_VECTOR (2 downto 0);

Y : out  STD_LOGIC_VECTOR (1 downto 0));

end FULLSUBTRACTOR_BEHAVIORAL_SOURCE;

architecture Behavioral of
FULLSUBTRACTOR_BEHAVIORAL_SOURCE is
```

```
begin
```

```
process (A)
```

```
begin
```

```
if (A = "001" or A = "010" or A = "111") then
```

```
Y <= "11";
```

```
elsif (A = "011") then
```

```
Y <= "01";
```

```
elsif (A = "100") then
```

```
Y <= "10";

else

Y <= "00";

end if;

end process;

end Behavioral;
```

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity full_sub_tb is

end entity;
```

```
architecture tb of full_sub_tb is

component FULLSUBTRACTOR_BEHAVIORAL_SOURCE is

Port ( A : in STD_LOGIC_VECTOR (2 downto 0);

Y : out STD_LOGIC_VECTOR (1 downto 0));

end component;


signal A: STD_LOGIC_VECTOR(2 downto 0);

signal Y: STD_LOGIC_VECTOR(1 downto 0);


begin


uut: FULLSUBTRACTOR_BEHAVIORAL_SOURCE port map(

A => A, Y => Y);


stim:process

begin

A <= "000";

wait for 20 ns;
```

```
A <= "001";
```

```
wait for 20 ns;
```

```
A <= "010";
```

```
wait for 20 ns;
```

```
A <= "011";
```

```
wait for 20 ns;
```

```
A <= "100";
```

```
wait for 20 ns;
```

```
A <= "101";
```

```
wait for 20 ns;
```

```
A <= "110";
```

```
wait for 20 ns;
```

```
A <= "111";

wait for 20 ns;

wait;

end process;

end tb;
```

2. Data flow Model Code:

-- Code your testbench here

library IEEE;

use IEEE.std_logic_1164.all;

entity tb_FULL_subtractor is

end tb_FULL_subtractor;

architecture myarch of tb_FULL_subtractor is

component FULL_subtractor is

port(

a: in std_logic;

b: in std_logic;

c: in std_logic;

s: out std_logic;


```

        cout: out std_logic;

    );

end component;

signal a,b,c: std_logic := '0';

signal s,cout: std_logic;

begin

    uut: FULL_subtractor port map(a,b,c,s,cout);


stim: process

begin

    a<='0';b<='0';c<='0'; wait for 100 ns;
    a<='0';b<='0';c<='1'; wait for 100 ns;
    a<='0';b<='1';c<='0'; wait for 100 ns;
    a<='0';b<='1';c<='1'; wait for 100 ns;
    a<='1';b<='0';c<='0'; wait for 100 ns;
    a<='1';b<='0';c<='1'; wait for 100 ns;
    a<='1';b<='1';c<='0'; wait for 100 ns;
    a<='1';b<='1';c<='1'; wait for 100 ns;

end process;

end myarch;


-- Code your design here

library IEEE;

use IEEE.std_logic_1164.all;


entity FULL_subtractor is

```

```

port(a: in std_logic;
     b: in std_logic;
     c: in std_logic;
     s: out std_logic;
     cout: out std_logic;
);
end FULL_subtractor;

```

architecture myarch of FULL_subtractor is


```
begin
```

```
    s<=a xor b xor c;
```

```
    cout<=(b and c) or ((not a) and ( b or c));
```

```
end myarch;
```

Output:

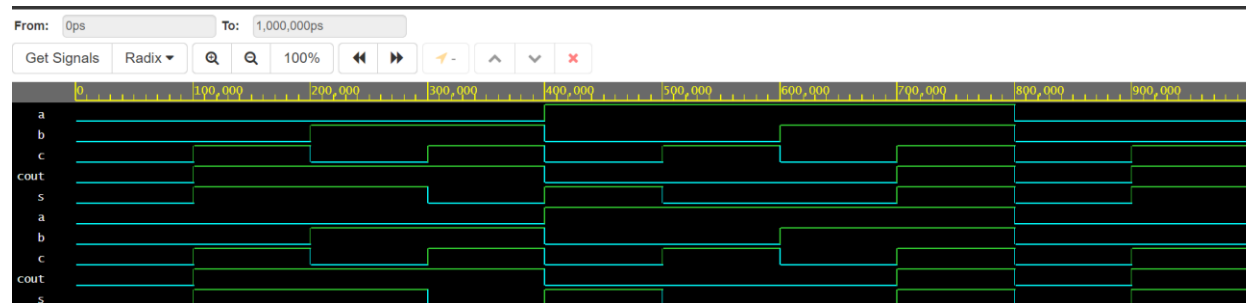

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Discussion:

Assignment 3: Implementation of 8 bit adder & 8 bit subtractor and 4 bit parallel Adder and Subtractor using XILINX ISE

Aim :

Software used:

Property Name	Xilinx ISE
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	VHDL

8 bit Adder:

Theory:

An **8 Bit Adder** is an electronic circuit, which adds 2 Binary values, each of size 8 Bits.

Data flow Model:

Here, the circuit is designed using the **Dataflow Architecture**, which takes into account, the **Boolean function**, of the circuit.

Code:

Data flow model code:

-- Code your testbench here

library IEEE;

use IEEE.std_logic_1164.all;

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;


ENTITY tb_uadder IS
END tb_uadder;


ARCHITECTURE behavior OF tb_uadder IS


    -- Component Declaration for the Unit Under Test (UUT)


    COMPONENT uadder
    PORT(
        A : IN  std_logic_vector(7 downto 0);
        B : IN  std_logic_vector(7 downto 0);
        C : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;


    --Inputs
    signal A : std_logic_vector(7 downto 0) := (others => '0');
    signal B : std_logic_vector(7 downto 0) := (others => '0');

```

```

--Outputs

signal C : std_logic_vector(7 downto 0);

-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

--constant <clock>_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)

    uut: uadder PORT MAP (

        A => A,

        B => B,

        C => C

    );

    -- Clock process definitions

    --<clock>_process :process

    --begin

        --<clock> <= '0';

        --wait for <clock>_period/2;

        --<clock> <= '1';

        --wait for <clock>_period/2;

    --end process;

```

```

-- Stimulus process

stim_proc: process
begin
    -- hold reset state for 100 ns.

    A<="00101111";B<="00110101"; wait for 100 ns;

    --wait for <clock>_period*10;

    -- insert stimulus here

    wait;

end process;

END;

-- Code your design here

library IEEE;
use IEEE.std_logic_1164.all;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if using

```

```
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

entity uadder is

```
Port ( A : in  STD_LOGIC_VECTOR (7 downto 0);
      B : in  STD_LOGIC_VECTOR (7 downto 0);
      C : out STD_LOGIC_VECTOR (7 downto 0));
```

end uadder;


architecture Dataflow of uadder is

begin

```
C <= A + B;
```

end Dataflow;

Output:

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

8 bit Subtractor:

Theory :

An **8-Bit Subtractor** is an electronic circuit which subtracts 2 Binary digits, each of size 8 Bits.

Data flow model:

Here, the circuit is designed using the **Dataflow Architecture**, which takes into account, the **Boolean function**, of the circuit.

Code: (Dataflow model code)

```
-- Code your testbench here
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```



```
--USE ieee.numeric_std.ALL;
```

```
ENTITY tb_uadder IS
```

```
END tb_uadder;
```

```
ARCHITECTURE behavior OF tb_uadder IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT uadder
```

```
PORT(
```

```
    A : IN  std_logic_vector(7 downto 0);
```

```
    B : IN  std_logic_vector(7 downto 0);
```

```
    C : OUT std_logic_vector(7 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic_vector(7 downto 0) := (others => '0');
```

```
signal B : std_logic_vector(7 downto 0) := (others => '0');
```

```
--Outputs
```

```
signal C : std_logic_vector(7 downto 0);
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
--constant <clock>_period : time := 10 ns;
```

```
BEGIN
```

```
    -- Instantiate the Unit Under Test (UUT)
```

```
uut: uadder PORT MAP (
```

```
    A => A,
```

```
    B => B,
```

```
    C => C
```

```
);
```

```
-- Clock process definitions
```

```
--<clock>_process :process
```

```
--begin
```

```
    --<clock> <= '0';
```

```
    --wait for <clock>_period/2;
```

```
    --<clock> <= '1';
```

```
    --wait for <clock>_period/2;
```

```
--end process;
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
begin
```

```
    -- hold reset state for 100 ns.
```

```

A<="00101111";B<="00110101"; wait for 100 ns;

--wait for <clock>_period*10;

-- insert stimulus here

wait;

end process;

END;

-- Code your design here

library IEEE;
use IEEE.std_logic_1164.all;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.

```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

entity uadder is

```
Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
```

```
      B : in STD_LOGIC_VECTOR (7 downto 0);
```

```
      C : out STD_LOGIC_VECTOR (7 downto 0));
```

```
end uadder;
```


architecture Dataflow of uadder is

begin

```
C <= A - B;
```

end Dataflow;

Output:

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

4 bit Parallel Adder:

Theory:

A **4 Bit Parallel Adder** is an electronic circuit, which adds 2 Binary values, each of size 4 Bits and provides the sum as the output.

Dataflow model:

Here, the circuit is designed using the **Dataflow Architecture**, which takes into account, the **Boolean function**, of the circuit.

Code:

-- Code your testbench here

library IEEE;

use IEEE.std_logic_1164.all;

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--USE ieee.numeric_std.ALL;

ENTITY tb_uadder IS

END tb_uadder;

ARCHITECTURE behavior OF tb_uadder IS

-- Component Declaration for the Unit Under Test (UUT)

```
COMPONENT uadder
```

```
PORT(
```

```
    A : IN  std_logic_vector(3 downto 0);
```

```
    B : IN  std_logic_vector(3 downto 0);
```

```
    C : OUT std_logic_vector(3 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic_vector(3 downto 0) := (others => '0');
```

```
signal B : std_logic_vector(3 downto 0) := (others => '0');
```

```
--Outputs
```

```
signal C : std_logic_vector(3 downto 0);
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
--constant <clock>_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: uadder PORT MAP (
```

```
    A => A,
```

```

        B => B,

        C => C

    );

-- Clock process definitions
--<clock>_process :process
--begin

    --<clock> <= '0';

    --wait for <clock>_period/2;

    --<clock> <= '1';

    --wait for <clock>_period/2;

--end process;


-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.

    A<="0010";B<="0011"; wait for 100 ns;

    --wait for <clock>_period*10;

    -- insert stimulus here

    wait;

end process;

```

```

END;

-- Code your design here

library IEEE;
use IEEE.std_logic_1164.all;


library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity uadder is
    Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
          B : in  STD_LOGIC_VECTOR (3 downto 0);
          C : out STD_LOGIC_VECTOR (3 downto 0));
end uadder;

```


architecture Dataflow of uadder is

begin

C <= A + B;

end Dataflow;

Output:



4 bit Parallel Subtractor:

Theory:

A **4 Bit Parallel Subtractor** is an electronic circuit, which subtracts 2 Binary values, each of size 4 Bits and provides the difference, as output.

Dataflow model:

Here, the circuit is designed using the **Dataflow Architecture**, which takes into account, the **Boolean function**, of the circuit.

Code :

-- Code your testbench here

library IEEE;

use IEEE.std_logic_1164.all;

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--USE ieee.numeric_std.ALL;

ENTITY tb_uadder IS

END tb_uadder;

ARCHITECTURE behavior OF tb_uadder IS

-- Component Declaration for the Unit Under Test (UUT)

```
COMPONENT uadder
```

```
PORT(
```

```
    A : IN  std_logic_vector(3 downto 0);
```

```
    B : IN  std_logic_vector(3 downto 0);
```

```
    C : OUT std_logic_vector(3 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic_vector(3 downto 0) := (others => '0');
```

```
signal B : std_logic_vector(3 downto 0) := (others => '0');
```

```
--Outputs
```

```
signal C : std_logic_vector(3 downto 0);
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
--constant <clock>_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: uadder PORT MAP (
```

```
    A => A,
```

```

        B => B,

        C => C

    );

-- Clock process definitions
--<clock>_process :process
--begin

    --<clock> <= '0';

    --wait for <clock>_period/2;

    --<clock> <= '1';

    --wait for <clock>_period/2;

--end process;


-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.

    A<="0111";B<="0010"; wait for 100 ns;

    --wait for <clock>_period*10;


    -- insert stimulus here


    wait;

end process;

```

END;

-- Code your design here

library IEEE;

use IEEE.std_logic_1164.all;

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx primitives in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity uadder is

Port (A : in STD_LOGIC_VECTOR (3 downto 0);

B : in STD_LOGIC_VECTOR (3 downto 0);

C : out STD_LOGIC_VECTOR (3 downto 0));

end uadder;


architecture Dataflow of uadder is

begin

C <= A - B;

end Dataflow;

Output :

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Discussion :

Assignment 4: Implementation of binary to Gray converter and Gray to Binary converter using XILINX ISE

Aim:

Software used:

Property Name	
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	

Gray to Binary:

Theory :

Truth table: (Gray to Binary)

Gray				Binary			
G3	G2	G1	G0	B3	B2	B1	B0

Dataflow Model:

Code:

Behavioral Model code:

Dataflow Model Code:

Output :

Binary to Gray:

Theory :

Truth table: (Binary to Gray)

Binary				Gray			
B3	B2	B1	B0	G3	G2	G1	G0

Dataflow Model:

Code:

Behavioral Model code:

Dataflow Model Code:

Output :

Discussion:

Assignment 5: Implementation of 4bit comparator, 2:4 Decoder,3:8 Decoder, 8bit Multiplier using XILINX ISE

Aim:

Software used:

Property Name	
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	

4 bit Comparator:

Theory:

Code:

Behavioral Model Code:

Output:

2:4 Decoder:

Truth table:

I1	I0	D3	D2	D1	D0

Dataflow Model:

Code:

Output :

3:8 Decoder:

Truth table:

I2	I1	I0	D7	D6	D5	D4	D3	D2	D1	D0

Dataflow Model:

Code:

Output :

8 Bit Multiplier:

Code:

Output:

Discussion:

Assignment 6: Implementation of 2:4 Decoder (using case), 4:2 Encoder (Dataflow & using case), 8:3 Encoder (using loop)

Aim:

Software used:

Property Name	
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	

2:4 Decoder:

Theory:

Truth table:

I1	I0	D3	D2	D1	D0

Behavioral Model: (using case)

Output :

4:2 Encoder:

Theory :

Truth Table:

I3	I2	I1	I0	E1	E0

Dataflow Model:

Dataflow Code:

Output :

Behavioral Code:

Output :

8:3 Encoder:

Truth Table:

I7	I6	I5	I4	I3	I2	I1	I0	E2	E1	E0

Behavioral Code:

Output :

Discussion :

Assignment 7: Implementation of 2:1 MUX(Dataflow), 4:1 MUX (Dataflow, if-else and using Case) and 1:4 Demux (Using Dataflow and case) using XILINX ISE.

Software used:

Property Name	
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	

Theory :

2:1 MUX:

Truth table:

INPUT			OUTPUT
S	I1	I0	M

Dataflow Model:

Code:

Dataflow Model:

Output :

4:1 MUX:

Truth Table:

INPUT						OUTPUT
S1	S0	I3	I2	I1	I0	M

Dataflow Model:

Code:

Dataflow Model Code:

Output :

Behavioral Model code: (Using CASE)

Behavioral Model code: (Using if-else)

Output:

1:4 De mux:

Theory :

Truth Table:

Data Input	Select Input		Output			
D	S1	S0	Y3	Y2	Y1	Y0

Dataflow Model:

Dataflow Code:

Behavioral code (using Case):

Output:

Discussion:

Assignment 8: Implementation of Full Adder using Half Adder (using Structural Method), 4 bit Parallel Adder (using Structural Method).

Aim :

Software used:

Property Name	
Device family	
Device	
Package	
Speed	

Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	

Full Adder:

Theory:

Truth Table:

INPUT			OUTPUT	
A	B	Cin	S	Cout

Structural Model

Code:

Output:

4 Bit Parallel Adder:

Theory:

Structural Model:

Code:

Output:

Discussion:

Assignment 9: Implementation of 2:1 MUX (using Structural Method) & 4:1 MUX using 2:1 MUX (using Structural Method) in XILINX ISE

Aim :

Software used:

Property Name	
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	

Theory :

2:1 MUX

Truth table:

INPUT			OUTPUT
S	I1	I0	Y

Structural Model:

Code : (Structural method)

Output :

4:1 MUX

Truth table:

S1	S0	Y

Structural Model:

Code : (Structural)

Output :

Discussion :

Assignment 10: Implementation of SR flip flop, JK flip flop, D flip flop, T flip flop (using if –else) in XILINX ISE

Aim :

Software used:

Property Name	
Device family	
Device	
Package	
Speed	
Top-level source type	
Synthesis Tool	
Simulator	
Preferred Language	

Theory :**SR flip flop:****Truth table:**

CLK	S	R	Q	Q'

Dataflow model:

Code :

Output :

JK flip flop:

Truth table:

CLK	J	K	Q	Q'

Dataflow model:

Code :

Output :

D flip flop:

Truth table:

CLK	D	Q	Q'

Dataflow model:

Code :

Output :

T flip flop:

Truth table:

CLK	T	Q	Q'

Dataflow model:

Code :

Output :

Discussion: